

**EEE 454**

**VLSI I**

**Project Group No: 8**

**Project Title : VLSI Design Project: Configurable Logic Block (CLB)**

**Prepared By:**

**Student Name: Prasun Datta**

**Student ID: 201606148**

**Name of Group Member: Ratul Kundu**

**Mahin Ahmed**

**Shahedul Hasan**

**Student ID of Group Member: 201606147**

**201606180**

**201606179**

**Date of Submission: 17/06/2021**

## **Introduction:**

In this project, a “Configurable Logic Block(CLB)” needs to be implemented. Particularly, 3:1 CLB is asked to design here. The components of the CLB is listed below.

- **LUT** : A look up table is like a mux which will perform some specified logical operation. In this case, it will perform NOR operation.
- **SRAM** : This will store the input values of the mux of the LUT. In our case total 8 SRAM cells need to be implemented since this is a 3: 1 CLB.
- **D Flip-flop**: Flip-flop will enable the CLB to perform sequencing operation. It will act like a memory element of the CLB block.
- **Mux** : In this design 2:1 mux will be implemented. Mux will basically show outputs based on the input select pins.

In the proposed design , following input & output pins will be implemented.

- ✓ **Clk** : This pin will be connected to the D flip-flop.
- ✓ **Load** : This pin will control the write and store operation of the SRAM.  
Load = 1 data will be written to the SRAM cells.  
Load = 0 data will be stored(previously written data) in the SRAM cells.
- ✓ **Data** : (7:0) Serial input of bit stream to load into the SRAM.
- ✓ **LUT Input Pins** : (2:0) Three select pins will be available as select pins of the mux placed inside the LUT block
- ✓ **Output Pin**: There will be a single output pin which will be the output port of the LUT block.

## **Project Implementation Details:**

<b>PC IP</b>	103.94.135.219:1324
<b>login</b>	vlsi08 (pw: vlsi08)
<b>Logic Family</b>	Pass Transistor
<b>Logic Function</b>	NOR(A,B,C)

### **Schematic of D Flip-flop Using Pass Transistor:**

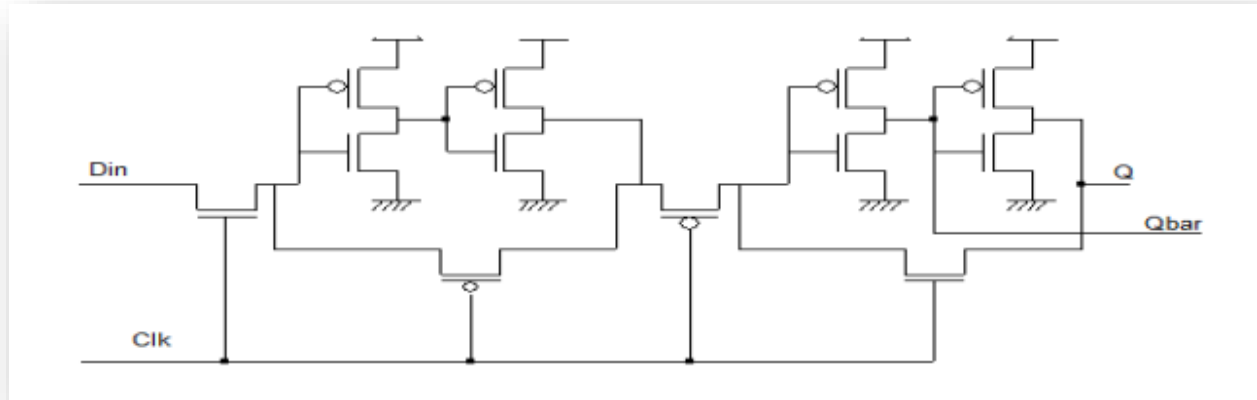


Fig 1 : D flip-flop implemented using pass transistor [1]

Here Din = data input pin of the flip-flop

Clk :clock pin of the flip-flop.

Q = output pin of the flip-flop

Qbar = inverted output of the flip-flop

### **Truth Table of the Flip-flop:**

D Flip Flop		
Input	Output	
D	Q	$Q^{\wedge}$
0	0	1
1	1	0

Fig 2: Truth table of D flip-flop [2]

### Schematic of Mux Using Pass-transistor:

 


Fig 3: 2:1 mux using pass transistor. [3]

Here S = Select pin of the mux

A & B = These are the input pins of the mux which will connect with Z based on the values of select pin. In our design A & B will come from two different SRAM cells.

### Truth Table:

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Table 1 : 2:1 mux truth table

### **Schematic of LUT:**

 


Fig 4 : 3:1 Look-up table

Here we will design the 2:1 mux using the pass transistor logic and the corresponding schematic is attached above. This will be basically an 8:1 mux which will be implemented with five 2:1 mux.

### **Design of SRAM Cell:**

Static random-access memory (static RAM or SRAM) is a type of random-access memory (RAM) that uses latching circuitry (flip-flop) to store each bit. SRAM is volatile memory; data is lost when power is removed. [4]

Here we will adopt the standard 6 transistor (6T) design of SRAM cell.

 


Fig 5 : 6T SRAM Cell [4]

A typical SRAM cell is made up of six MOSFETs. Each bit in an SRAM is stored on four transistors (M1, M2, M3, M4) that form two cross-coupled inverters. This storage cell has two stable states which are used to denote **0** and **1**. Two additional access transistors serve to control the access to a storage cell during read and write operations. For our design,

WL = word pin.

WL = 1 ; the write cycle begins by applying the value to be written to the bit lines

WL = 0 ; the read cycle is started.

BL = bit lines ; through this line expected bit will be sent to the SRAM cell.

### **Schematic of Single Unit of CLB:**

Assembling all of the above elements our CLB unit will look something like this.

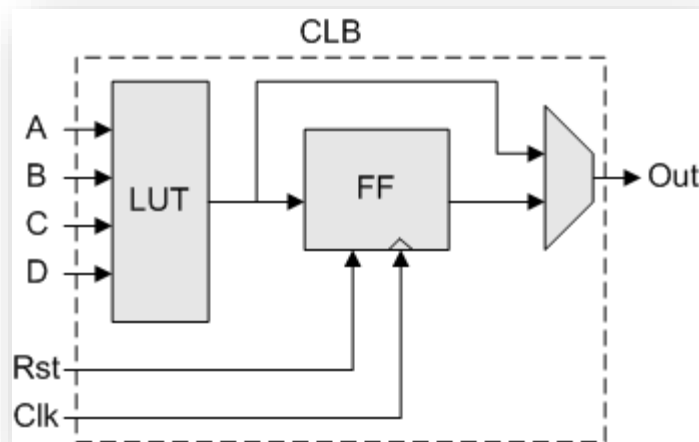


Fig 6: Whole picture of CLB block. [5]

In our case there will be 3 inputs and reset signal will not be incorporated.

### **Schematic Design of Proposed CLB:**

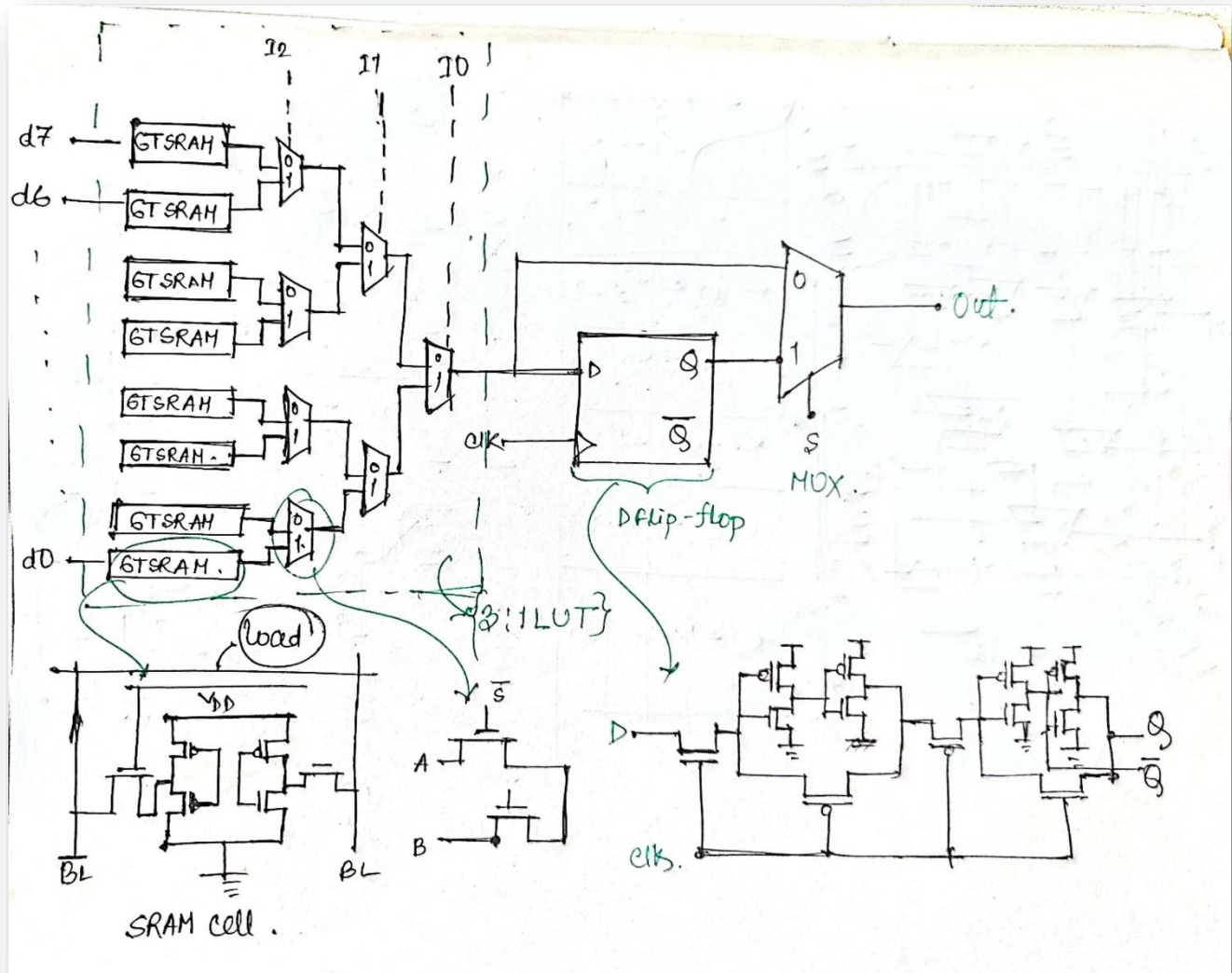


Fig 7: Whole diagram of proposed CLB

## Work Division:

Members Name	Assigned Work
Prasun Datta	SRAM Design
Ratul Kundu	Mux Design
Mahin Ahmed	LUT Design
Shahedul Hasan	Flip-flop Design



## References

- [1] M. J. R. a. S. Malarkann, "LEAKAGE POWER REDUCTION AND ANALYSIS OF CMOS SEQUENTIAL CIRCUITS," *International Journal of VLSI design & Communication Systems (VLSICS)*, 2012.
- [2] "D Flip Flop PLC Ladder Logic," [Online]. Available: <https://instrumentationtools.com/plc-program-to-implement-d-flip-flop-in-plc/>.
- [3] "Shakshat Virtual Lab," [Online]. Available: [https://vlsi-iitg.vlabs.ac.in/Multiplexer\\_theory.html](https://vlsi-iitg.vlabs.ac.in/Multiplexer_theory.html).
- [4] "Static random-access memory," [Online]. Available: [https://en.wikipedia.org/wiki/Static\\_random-access\\_memory#/media/File:SRAM\\_Cell\\_\(6\\_Transistors\).svg](https://en.wikipedia.org/wiki/Static_random-access_memory#/media/File:SRAM_Cell_(6_Transistors).svg).
- [5] "FPGAKey," [Online]. Available: <https://www.fpgakey.com/wiki/details/51>.